

COURSE CODE(CREDITS): 18B11EC212(4)

MAX. MARKS: 35

COURSE NAME: Basic Electrical Science

COURSE INSTRUCTORS: Dr. Alok Kumar

MAX. TIME: 2 Hours

*Note: (a) All questions are compulsory.*

*(b) Marks are indicated against each question in square brackets.*

*(c) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems*

**Q.1** Find the current in  $3\Omega$  resistance using superposition theorem in the given Fig.1.

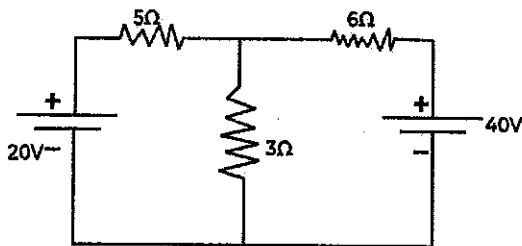


Fig.1

[CO1] [4 Marks]

**Q.2** How do biomedical signals differ from other types of signals? Explain the importance of biomedical signal processing in healthcare. [CO5] [4Marks]

**Q.3** Explain the different waves and intervals observed in a typical ECG waveform. Discuss emerging technologies and advancements in ECG monitoring and interpretation. [CO5] [4 Marks]

**Q.4** Find the average value, RMS value, form factor and peak factor of the waveform shown In Fig.2

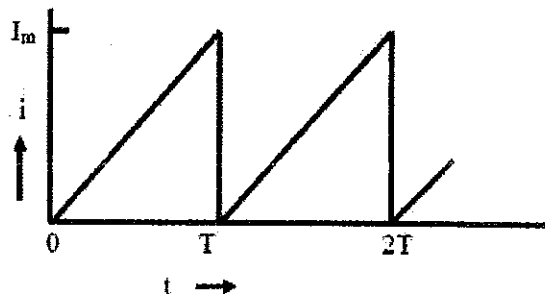


Fig.2

[CO2, CO3] [4 Marks]

**Q.5** What are the main components of a transformer, and how do they contribute to its operation? [CO4] [4 Marks]

**Q.6** What are the clinical indications for MRI, and in which scenarios is it preferred over CT? [CO5] [3Marks]

**Q.7** A 100-kVA, 2400/240-V, 60-Hz step-down transformer (ideal) is used between a transmission line and a distribution system.

- Determine turns ratio.
- What secondary load impedance will cause the transformer to be fully loaded, and what is the corresponding primary current?
- Find the load impedance referred to the primary. [CO4] [3 Marks]

**Q.8** In the given Fig. 3, find the following.

- equation for current  $i(t)$ ,
  - value of current at time  $t=0.1$  sec,
  - analyze the response.
- Consider the value of voltage source and other components as follows:  $v_s=20V$ ,  $R=9\Omega$ ,  $L=1H$ , and  $C=.05F$ .

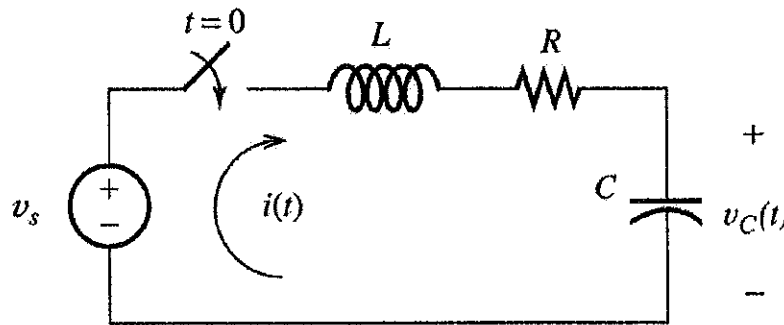


Fig.3

[CO2, CO3] [5 Marks]

**Q.9** Find the current  $i(t)$  in the circuit shown in Fig.4. Consider the  $V_s = 40\sin(3000t)V$

[CO3] [4 Marks]

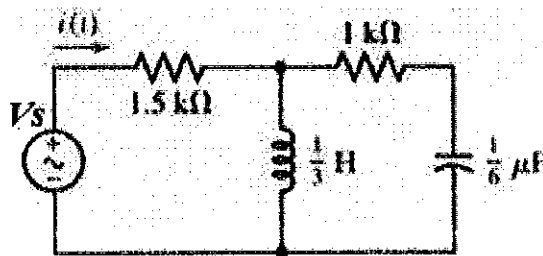


Fig.4