

COURSE CODE (CREDITS): 18B11EC313 (4)

MAX. MARKS: 15

COURSE NAME: ELECTRONIC DEVICES AND CIRCUITS

COURSE INSTRUCTORS: Dr. Shruti Jain

MAX. TIME: 1 Hour

*Note: (a) All questions are compulsory.*

*(b) Marks are indicated against each question in square brackets.*

*(c) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems.*

**Section A (Short Answers :  $1 \times 5 = 5$  marks) [CO1]**

1.

- i. Total hole current is a sum of \_\_\_\_\_ and \_\_\_\_\_ current. Write formulas too.
- ii. How Fermi level in a p-type semiconductor is a function of acceptor concentration.
- iii. What is the significance of operating point and load line. How Sita can calculate for diode?
- iv. What is the difference between different types of resistances of diode?
- v. How Shyam can evaluate maximum zener current and minimum current limit resistance?

**Section B (Long Answers :  $2 \times 5 = 10$  marks) [CO1]**

2. Chirag is working on the positive biased clipping circuit with 10V peak to peak input sinusoidal waveform as input with 1 V biasing. What is the expected output?
3. "Zener diode as a Voltage Regulator". Justify this statement.
4. Determine the donor concentration in an n-type germanium semiconductor having a conductivity of  $2.016 \text{ (ohm m)}^{-1}$ , if the mobility of electrons in germanium is about  $0.23 \text{ m}^2/\text{V-s}$ . Also, determine the minority carrier density. Assume  $n_i = 2.5 \times 10^{19}/\text{m}^3$ .



5. The reverse saturation current of a silicon PN junction diode is  $10\mu\text{A}$  at the temperature  $300\text{K}$ . Determine the forward bias voltage to be applied across the PN junction to obtain a current of about  $100\text{mA}$ .
6. Complete the table below :

	Half wave rectifier	Centre tapped Full wave rectifier	Full wave bridge rectifier
Number of diodes	01		
Peak inverse voltage		$2 V_m$	
Average DC output voltage	$V_m/\pi$		
RMS output voltage	$V_m/2$		