

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -3 EXAMINATION- 2024

MSc (Physics)

COURSE CODE (CREDITS): 24MS3PH301

MAX. MARKS: 35

COURSE NAME ELECTRONICS-II

COURSE INSTRUCTORS: SKK

MAX. TIME: 2 Hours

Note: (a) All questions are compulsory.

(b) All questions carry equal marks

1. Sketch the circuit diagram of Weighted Resistor D/A Converter. Explain its working with input output table.
2. Explain the successive approximation of A/D converter with example.
3. An 8 bit D/A converter provides analog output which has a maximum value of 10V. the output may have an error of ΔV due to drift in component values, temperature etc, how large can ΔV be before the least significant bit would no longer be significant?
4. What is difference between A/D converter using voltage to frequency conversion and voltage to time conversion.
5. For a memory M words storage, find the number pins required for addressing and the address range in binary format for each of the following cases M=4, 16, 64, 256, 1024
6. Explain the working of charge coupled device (CCD) memory
7. Draw a 16-bit ROM array and explain its working