

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -1 EXAMINATION- 2025

B.Tech-I Semester (CSE/IT/ECE/CE)

COURSE CODE (CREDITS): 24B11EC211(4) / 18B11EC211 (4)

MAX. MARKS: 15

COURSE NAME: Basic Electrical Engineering/ Electrical Sciences



COURSE INSTRUCTORS: Dr. Rajiv, Dr. Shweta, Dr. Salman, Dr. Harsh, Dr. Nishant, Lt. Pragya




MAX. TIME: 1 Hour

Note: (a) All questions are compulsory.

(b) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

(c) Scientific calculator is allowed.

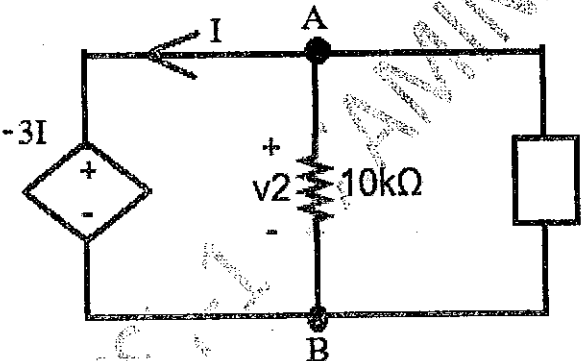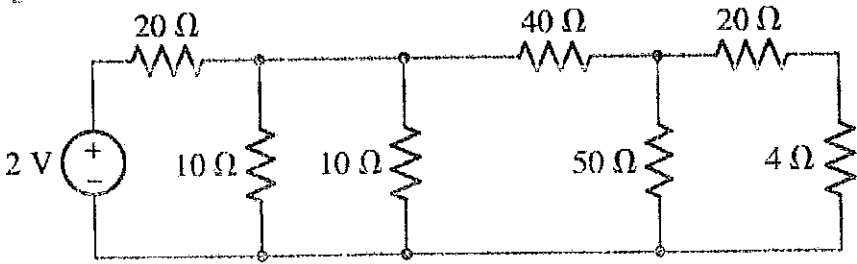Q.No	Question	CO	Marks
Q1	<p>(a) For the circuit given below, what value of I is required for the dependent source to be supplying 12W?</p> <p>(b) Determine the value of v_2.</p> <p>(c) Determine the magnitude and the direction of the current flowing through the $10\text{ k}\Omega$ resistor.</p> 	CO1	3
Q2	<p>With regard to the circuit shown below, using only current division/voltage division rule, determine the power dissipated by the 4Ω resistor.</p> 	CO1	3
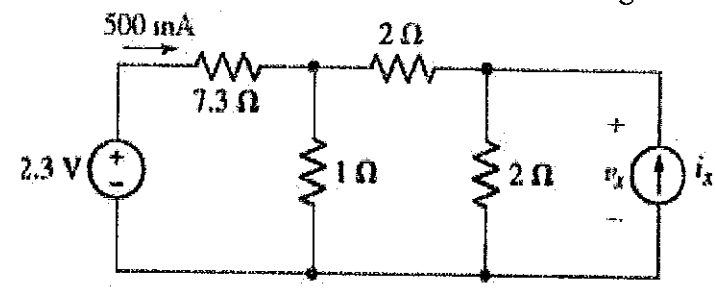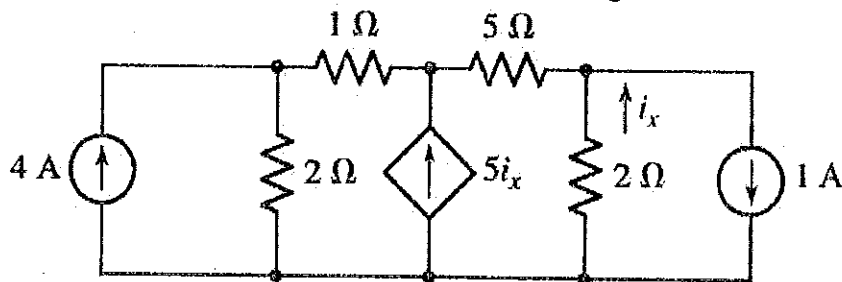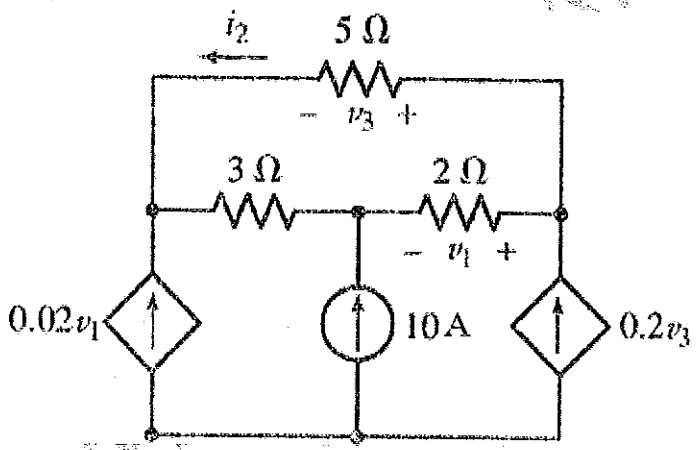
<p>Q3.</p>	<p>Determine the value of v_x as labeled in the circuit given below:</p> 	<p>CO1</p>	<p>3</p>
<p>Q4</p>	<p>Using nodal analysis, determine i_x in the following circuit:</p> 	<p>CO2</p>	<p>3</p>
<p>Q5</p>	<p>Determine the current i_2 as labeled in the circuit below, using mesh analysis.</p> 	<p>CO2</p>	<p>3</p>