

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT  
 TEST 1 EXAMINATION - September 2017  
 B.Tech 1<sup>st</sup> Semester (ECE, CSE, IT & CE)


COURSE CODE: 10B11EC111  
 COURSE NAME: Electrical Circuit Analysis  
 COURSE CREDITS: 4

MAX. MARKS: 15  
 MAX. TIME: 1HR

*Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.*

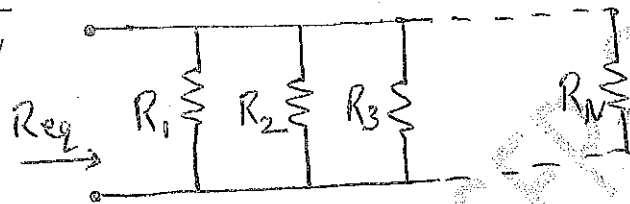
Q1. (a) Prove that the equivalent resistance of N resistors connected in parallel is given by

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$




(2)

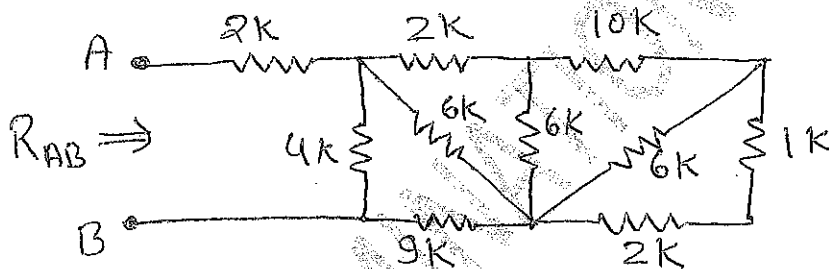(b) Determine the equivalent resistance between terminals A-B in the network shown below. (3)



Q2. (a) Define open circuit and short circuit. What is the resistance for each? (2)

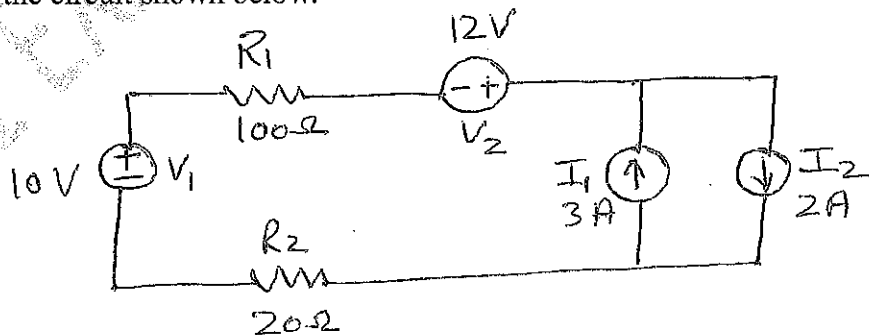(b) Find the power consumed or delivered by the Voltage sources  $V_1$  &  $V_2$ , Current sources  $I_1$  &  $I_2$  and Resistors  $R_1$  &  $R_2$  in the circuit shown below. (3)



Q3. (a) Define Node. What is Kirchhoff's Current Law? (2)

(b) Using Nodal analysis compute the voltage across each current source. (3)

