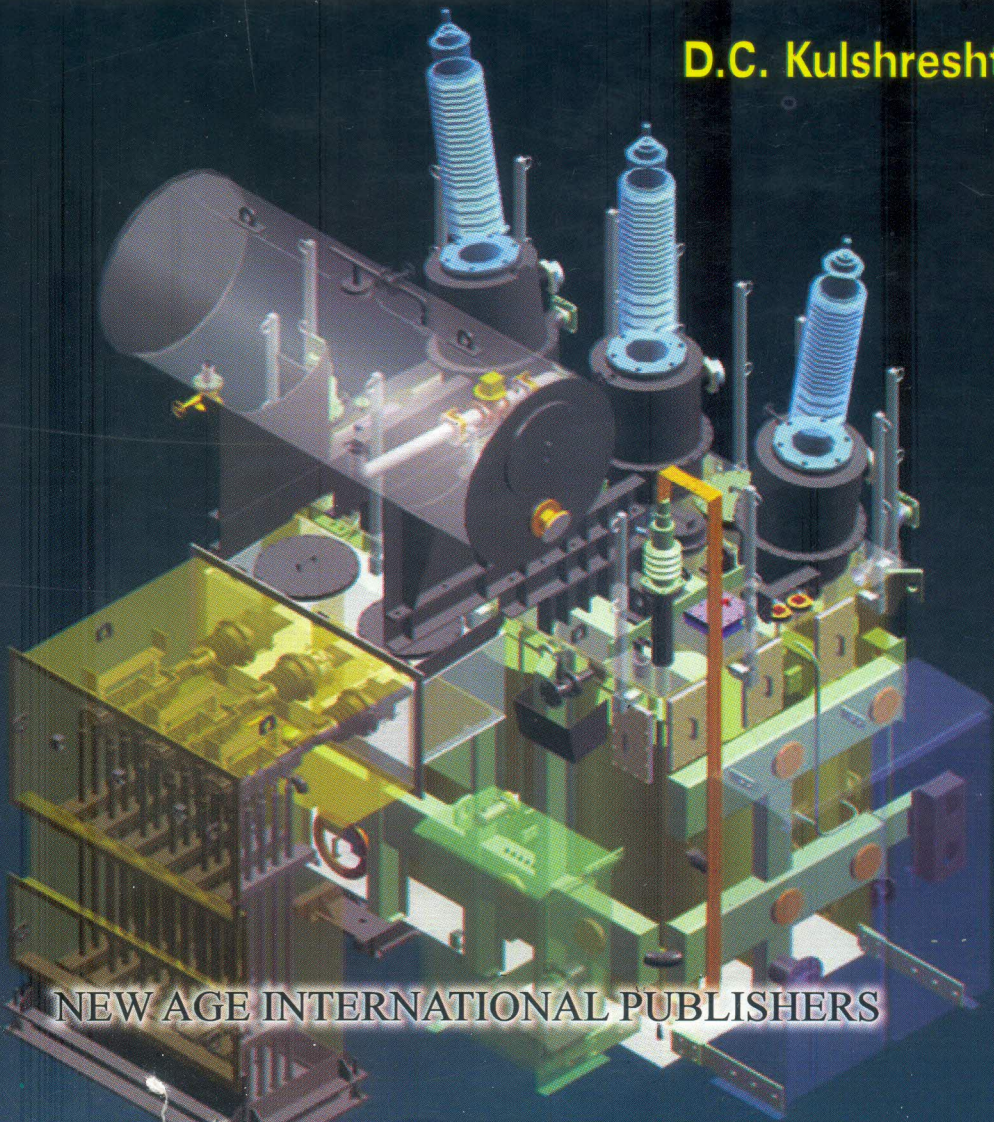


NEW AGE

REVISED SECOND EDITION

ELECTRONIC DEVICES AND CIRCUITS


D.C. Kulshreshtha



NEW AGE INTERNATIONAL PUBLISHERS

ELECTRONIC DEVICES AND CIRCUITS

REVISED SECOND EDITION

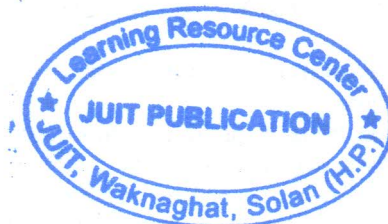

D.C. Kulshreshtha

Professor

Dept. of Electronics and Communication Engineering
Jaypee University of Information Technology,
Wahnaghat, Distt. : Solan (HP)-173 215

Formerly at

Department of Electronics Engineering
Delhi College of Engineering, Delhi



PUBLISHING FOR ONE WORLD

NEW AGE INTERNATIONAL (P) LIMITED, PUBLISHERS

New Delhi • Bangalore • Chennai • Cochin • Guwahati • Hyderabad
Jalandhar • Kolkata • Lucknow • Mumbai • Ranchi

Visit us at www.newagepublishers.com

Copyright © 2006, 2004, New Age International (P) Ltd., Publishers

Published by New Age International (P) Ltd., Publishers

First Edition: 2004

Second Edition: 2006

Reprint: 2010

All rights reserved.

No part of this book may be reproduced in any form, by photostat, microfilm, xerography, or any other means, or incorporated into any information retrieval system, electronic or mechanical, without the written permission of the copyright owner.

Branches:

- No. 37/10, 8th Cross (Near Hanuman Temple), Azad Nagar, Chamrajpet, **Bangalore**- 560 018.
Tel.: (080) 26756823, Telefax: 26756820, E-mail: bangalore@newagepublishers.com
 - 26, Damodaran Street, T. Nagar, **Chennai**- 600 017. Tel.: (044) 24353401, Telefax: 24351463
E-mail: chennai@newagepublishers.com
 - CC-39/1016, Carrier Station Road, Ernakulam South, **Cochin**- 682 016. Tel.: (0484) 2377004, Telefax: 4051303
E-mail: cochin@newagepublishers.com
 - Hemsan Complex, Mohd. Shah Road, Paltan Bazar, Near Starline Hotel, **Guwahati**- 781 008. Tel.: (0361) 2513881
Telefax: 2543669, E-mail: guwahati@newagepublishers.com
 - No. 105, 1st Floor, Madhiray Kaveri Tower, 3-2-19, Azam Jahi Road, Nimboliadda, **Hyderabad**- 500 027.
Tel.: (040) 24652456, Telefax: 24652457, E-mail: hyderabad@newagepublishers.com
 - RDB Chambers (Formerly Lotus Cinema)106A, 1st Floor, S.N. Banerjee Road, **Kolkata**- 700 014.
Tel.: (033) 22273773, Telefax: 22275247, E-mail: kolkata@newagepublishers.com
 - 16-A, Jopling Road, **Lucknow**- 226 001. Tel.: (0522) 2209578, 4045297, Telefax: 2204098
E-mail: lucknow@newagepublishers.com
 - 142C, Victor House, Ground Floor, N.M. Joshi Marg, Lower Parel, **Mumbai**- 400 013. Tel.: (022) 24927869
Telefax: 24915415, E-mail: mumbai@newagepublishers.com
 - 22, Golden House, Daryaganj, **New Delhi**- 110 002. Tel.: (011) 23262370, 23262368, Telefax: 43551305
E-mail: sales@newagepublishers.com
-

ISBN (10) : 81-224-1857-0

ISBN (13) : 978-81-224-1857-6

Rs. 295.00

C-10-04-4436

Printed in India at Print Perfect, Delhi.

Typeset at Innovative, Delhi

PUBLISHING FOR ONE WORLD

NEW AGE INTERNATIONAL (P) LIMITED, PUBLISHERS

4835/24, Ansari Road, Daryaganj, New Delhi-110002

Visit us at www.newagepublishers.com

Contents

<i>Foreword</i>	v
<i>Preface to the Second Edition</i>	vii
<i>Acknowledgement</i>	ix
1. Introduction to Electronics	1-23
1.1 What is Electronics	1
1.2 History of Electronics	2
The Transistor Era, Invention of the Integrated Circuits (IC), The Field-Effect Transistor (FET), Digital Integrated Circuits, Analog Integrated Circuits	
1.3 Applications of Electronics	3
(1) Communications and Entertainment, (2) Controls and Instrumentation, (3) Defence Applications, (4) Industrial Applications, (5) Medical Sciences, (6) Automobile Industry	
1.4 The Future	4
1.5 Electronic Circuit Components	5
Active Components, Passive Components	
<i>Resistors</i> : Fixed Resistors, Resistance Colour Coding, Variable Resistors, Some Special Resistors, Thermistor, LDR and VDR	
<i>Inductors</i> : Filter Chokes, Audio Frequency Chokes (AFC)	
<i>Capacitors</i> : Mica Capacitors, Ceramic Capacitors, Paper Capacitors, Electrolytic Capacitors, Variable Capacitors	
1.6 Voltage and Current Dividers	15
Voltage Divider, Current Divider	
1.7 Sources of Electrical Power	15
Ideal Voltage Source, Practical Voltage Source, Ideal Current Source, Practical Current Source, Equivalence between Voltage Source and Current Source	
1.8 Signals	21
1.9 SI Units	22
Some Derived Units, SI Prefixes	
<i>Another Unit of Energy</i> : The Electron Volt	
<i>Review Questions</i>	23

2. Semiconductor Physics	24-50
2.1 Why Study Semiconductor Physics	24
2.2 What are Semiconductors	25
2.3 Atomic Structure	25
Simplified Representation of Atoms	
2.4 Intrinsic Semiconductors	28
Crystal Structure of Semiconductors,	
Charge Carriers in Intrinsic Semiconductors,	
Carrier Concentration, Random Movement of Carriers,	
Hole as a Particle, Recombination of Electrons and Holes	
2.5 Electrical Conduction in Good Conductors	32
Drift Velocity, Conductivity of a Conductor	
2.6 Conduction in Intrinsic Semiconductors	34
Drift Current in Intrinsic Semiconductors,	
Conductivity of Intrinsic Semiconductors,	
Effect of Temperature on Conductivity	
2.7 Energy Bands in Solids	36
Energy Bands, Why Materials have Different Conductivities,	
Generation of Electron-Hole Pairs in Semiconductors,	
Fermi Energy Level	
2.8 Extrinsic Semiconductors	40
<i>N</i> -type, or Donor Type Semiconductor,	
Representation of <i>N</i> -type Semiconductor,	
<i>P</i> -type or Acceptor Type Semiconductor,	
Representation of <i>P</i> -type Semiconductor,	
Charge-carrier Concentration,	
Effect of Temperature on Extrinsic Semiconductor	
2.9 Diffusion Current	44
<i>Summary</i>	45
<i>Check Your Understanding</i>	47
<i>Review Questions</i>	48
<i>Multiple Choice Questions</i>	49
<i>Problems</i>	50
3. Semiconductor Diodes	51-114
3.1 <i>PN</i> -Junction Diode	51
Unidirectional Property of a <i>PN</i> -junction Diode, <i>PN</i> -Junction with no	
External Voltage Applied, Mechanism of Current Flow in a <i>PN</i> -Junction,	
<i>PN</i> -Junction with Forward Bias, <i>PN</i> -Junction with Reverse Bias,	
Summary of Biasing Conditions, Reverse Breakdown	
3.2 Transition and Diffusion Capacitances	57
3.3 <i>V-I</i> Characteristics	58
Silicon Diode versus Germanium Diode, How Temperature affects	
Semiconductor Diodes	

3.4	Diode Resistance	60
	Static or DC Resistance, Dynamic or AC Resistance	
3.5	Diode Equation	64
	Dynamic Resistance of a Diode	
3.6	Ideal Diode	65
	Circuit Model of a Diode, Simplified Circuit Model of a Diode	
3.7	Block Diagram of a DC Power Supply	69
3.8	Use of Diodes in Rectifier Circuits	70
	Half-wave Rectifier, Full-wave Rectifier, Centre-tap Rectifier, Bridge Rectifier	
3.9	Ratings of Rectifier Diodes	73
3.10	Figures of Merit of a Rectifier	75
	Ripple Factor, Rectification Efficiency, Performance of Half-wave Rectifier, Performance of Full-wave Rectifier	
3.11	How to Reduce Ripples in DC Output	80
	Shunt Capacitor Filter, Series Inductor Filter, Chok-Input LC Filter, Bleeder Resistor	
3.12	Zener Diode	84
3.13	A Simple Voltage Regulator	85
	Analysis of Zener Voltage Regulator Circuit, Important Specifications of Zener Diode	
3.14	Types of Diodes	89
	Signal Diodes, Power Diodes, Varactor Diodes, Point-Contact Diode, Schottky Diode, Tunnel Diode	
	<i>Summary</i>	92
	<i>Check Your Understanding</i>	94
	<i>Review Questions</i>	95
	<i>Multiple Choice Questions</i>	96
	<i>Problems</i>	100
	<i>Experimental Exercises</i>	
3.1	Semiconductor Diode Characteristics	103
3.2	Zener Diode Characteristics	105
3.3	Half-wave Rectifier	108
3.4	Full-wave Rectifiers	110
3.5	Filter Circuits	113
4.	Bipolar Junction Transistors (BJTs)	115-154
4.1	Introduction	115
4.2	BJT Structure	116
	Biasing Conditions of a Transistor	
4.3	Working of a Transistor	117
	Transistor Current Equation, Collector Reverse Leakage Current (I_{CBO}), Collector Current in Normal Operation, DC Alpha (α_0) of a Transistor, Other Biasing Conditions	

4.4	The Three Configurations	121
4.5	A Simple Common-Base Amplifier	123
4.6	Standard Notation for Symbols	124
4.7	Transistor Characteristics	125
4.8	CB Characteristics	125
	CB Input Characteristics, CB Output Characteristics	
4.9	CE Configuration	127
	Current Relations in CE Configuration, How Beta of a Transistor is Related to Its Alpha	
4.10	CE Characteristics	130
	CE Input Characteristics, CE Output Characteristics, Early Voltage	
4.11	CC Configuration	133
	Current Relations in CC Configuration	
4.12	Comparison between the Three Configurations	135
	Loading Effect	
4.13	Basic CE Amplifier Circuit	137
	DC Load Line, Amplifier Analysis Using DC Load Line	
	<i>Summary</i>	140
	<i>Check Your Understanding</i>	142
	<i>Review Questions</i>	143
	<i>Multiple Choice Questions</i>	143
	<i>Problems</i>	145
	<i>Experimental Exercise</i>	
4.1	BJT CB Characteristics	146
4.2	BJT CE Characteristics	150
5.	Field-Effect Transistors (FETs)	155-183
5.1	Introduction	155
5.2	Junction Field-Effect Transistor (JFET)	156
	Construction, Circuit Symbol, Analogy between a BJT and a JFET Why the Channel is so named, Working Principle of a JFET	
5.3	JFET Characteristics	159
	JFET Output Characteristics, JFET Transfer Characteristics	
5.4	Metal-Oxide Semiconductor FETs	163
5.5	Depletion-Type MOSFET (DE MOSFET)	163
	Structure, Working Principle of a DE MOSFET, Circuit Symbol, DE MOSFET Output Characteristics, DE MOSFET Transfer Characteristics	
5.6	Enhancement-Type MOSFET (EN MOSFET)	167
	Structure, Formation of Channel, What Happens on Applying v_{DS} Drain Characteristics of EN MOSFET, Circuit Symbol, Transfer Characteristic of EN MOSFET, Temperature Effects, The P-Channel MOSFET	
5.7	Complementary MOS (CMOS)	171
	VMOS Technology	

5.8	Comparison of FET with BJT How MOSFETs are Better than JFETs	172
5.9	FET Parameters	173
	<i>Summary</i>	175
	<i>Check Your Understanding</i>	177
	<i>Review Questions</i>	178
	<i>Multiple Choice Questions</i>	178
	<i>Problems</i>	179
	<i>Experimental Exercise</i>	
5.1	JFET Characteristics	180

6. Transistor Biasing and Stabilization 184-223

6.1	Need of Biasing a Transistor	184
6.2	Choice of Operating Region	184
6.3	Selection of the Operating Point	185
6.4	Need for Bias Stabilization	188
6.5	The Simplest Biasing Circuit	189
6.6	Base Bias or Fixed Bias Circuit Analysis of Fixed Bias Circuit, The Saturation Point, Why Fixed Bias Circuit not Used	190
6.7	Collector-to-Base Bias Circuit What is Negative Feedback, Analysis of Collector-to-Base Bias Circuit, Why Collector-to-Base Bias Circuit is Seldom Used	194
6.8	Emitter-Feedback Bias Circuit Analysis of Emitter-Feedback Bias Circuit, Drawbacks of Emitter-Feedback Bias Circuit	197
6.9	Emitter-Bias Circuit Analysis of Emitter-Bias Circuit, Why is the Emitter-Bias Circuit Immune to Changes in Current Gain	201
6.10	Voltage-Divider Bias Circuit Approximate Analysis, Checking the Assumption, Stabilization of Q-Point, More Accurate Analysis	203
6.11	Two-Supply Emitter-Bias Circuit Approximate Analysis, Accurate Analysis	208
6.12	Biasing the FET Biasing JFETs, Bias Stabilization for JFET, Biasing MOSFETs	209
	<i>Summary</i>	212
	<i>Check Your Understanding</i>	213
	<i>Review Questions</i>	214
	<i>Multiple Choice Questions</i>	214
	<i>Problems</i>	216
	<i>Experimental Exercises</i>	218
6.1	Fixed-Bias Circuit (with and without Emitter Resistor)	218
6.2	Voltage-Divider Bias Circuit	221

7. Small-Signal Single-Stage Amplifier	224-272
7.1 What is Meant by Amplification ? How an Electronic Amplifier is Different from a Step-up Transformer, Types of Electronic Amplifiers	224
7.2 The Gain of an Amplifier Ideal Voltage Amplifier	226
7.3 Single-Stage BJT Amplifier	226
7.4 The Capacitors Coupling Capacitor, Bypass Capacitor, Critical Frequency, High Frequency Border	227
7.5 Analysis of a BJT Amplifier	232
7.6 A Practical CE Amplifier Working of the Circuit, DC Analysis, AC Analysis, Is Collector AC Resistance Same as DC Resistance? Are We Ready for AC Analysis?	232
7.7 Graphical Method of AC Analysis AC Loadline, Loss of Signal at the Input, To Find the Output Voltage, The Voltage Gain, The Phase Reversal, The Current Gain	236
7.8 AC Equivalent Circuit Model of a BJT Hybrid Parameters of a BJT, h -parameter Circuit-Model of a BJT, Simplified h -parameter Model, Hybrid- π Circuit-Model of a BJT, How g_m is Related to other Parameters, Determining Hybrid- π Model Parameters	239
7.9 Equivalent Circuit Method of AC Analysis AC Analysis using h -parameter Model, AC Analysis using Hybrid- π Model, How Small is Small	244
7.10 FET Small-Signal Amplifier AC Analysis of FET Amplifier	251
7.11 FET Parameters AC Equivalent Circuit-Model of an FET, AC Equivalent of FET Amplifier Circuit	253
<i>Summary</i>	258
<i>Check Your Understanding</i>	259
<i>Review Questions</i>	260
<i>Multiple Choice Questions</i>	260
<i>Problems</i>	262
<i>Experimental Exercise</i>	
7.1 Single-stage CE BJT Amplifier	265
7.2 Single-stage FET Amplifier	269
8. Multistage Amplifiers	273-322
8.1 Why Do We Need Multistages	273
8.2 Voltage Gain of a Multistage Amplifier Gain in Decibels, Voltage Gain in dB, Why Use dB	274
8.3 Different Coupling Schemes Loading Effect in Multistage Amplifiers, RC Coupled Amplifier, LC and Transformer Coupling, Direct Coupling	277

8.4	Frequency Response of an RC Coupled Amplifier Bandwidth of an Amplifier, Why is the Limit Set at $0.707A_m$, Why Logarithmic Scale for Frequency, Why the Gain Falls in Low-frequency Range, Why the Gain Falls in High-Frequency Range, Effect on Bandwidth when Stages are Cascaded	284
8.5	Analysis of Two-stage RC Coupled Amplifier Two-Stage FET RC Coupled Amplifier, Two-Stage BJT RC Coupled Amplifier	291
8.6	Difference Amplifier	300
8.7	Distortion in Amplifiers (1) Frequency Distortion, (2) Phase or Delay Distortion, (3) Harmonic Distortion, Noise in Amplifiers	301
8.8	Classification of Amplifiers Classification Based on DC Bias	304
	<i>Summary</i>	308
	<i>Check Your Understanding</i>	310
	<i>Review Questions</i>	311
	<i>Multiple Choice Questions</i>	312
	<i>Problems</i>	313
	<i>Experimental Exercise</i>	
8.1	Gain of Two-Stage RC Coupled Amplifier	314
8.2	Frequency Response of Two-Stage RC Coupled Amplifier	317
9.	Power Amplifiers	323-360
9.1	Need for a Power Amplifier	323
9.2	How a Power Amplifier Differs from a Voltage Amplifier	324
9.3	A Simple Power Amplifier	324
9.4	How to Avoid Power Loss in R_C	325
9.5	Transformer-Coupled Single-Ended Power Amplifier Maximum Power Transfer Theorem, Transformer Impedance Matching	326
9.6	Power Considerations Output Circuit Efficiency, Heat Sinks	328
9.7	Analysis of a Single-ended Power Amplifier	330
9.8	Maximum Theoretical Efficiency Class-B Amplifier	333
9.9	Harmonic Distortion in Power Amplifiers	336
9.10	Push-pull Amplifier Why the Name "Push-Pull", Distortion in Push-Pull Amplifier Advantages of a Push-Pull Amplifier	338
9.11	Class-B Push-pull Amplifier Circuit Operation, Crossover Distortion How to Remove Crossover Distortion	343
9.12	Driver Stages Phase Inverter Circuit	345
9.13	Complementary Symmetry Push-pull Circuits Integrated-Circuit Power Amplifier	346

<i>Summary</i>	349
<i>Check Your Understanding</i>	350
<i>Review Questions</i>	351
<i>Multiple Choice Questions</i>	352
<i>Problems</i>	353
<i>Experimental Exercise</i>	
9.1 Single-ended Power Amplifier	354
9.2 Push-Pull Power Amplifier	357
10: Feedback in Amplifiers	361-390
10.1 Basic Concept of Feedback in Amplifiers	361
10.2 Types of Feedback	363
10.3 Voltage Gain of a Feedback Amplifier	365
10.4 Why Negative Feedback is Preferred	370
10.5 Effects of Negative Feedback on Amplifier Characteristics	370
(1) Negative Feedback Decreases the Sensitivity of the Amplifier Gain	
(2) Negative Feedback Increases the Input Resistance of the Amplifier	
(3) Negative Feedback Decreases the Output Resistance of the Amplifier	
(4) Negative Feedback Increases the Bandwidth of the Amplifier	
(5) Negative Feedback Reduces Distortion and Noise	
10.6 Typical Amplifier Circuits with Negative Feedback	376
An FET Amplifier using Series-Voltage Feedback, RC-Coupled	
Amplifier without Bypass Capacitor, Emitter Follower Circuit	
<i>Summary</i>	379
<i>Review Questions</i>	380
<i>Check Your Understanding</i>	381
<i>Multiple Choice Questions</i>	382
<i>Problems</i>	383
<i>Experimental Exercise</i>	
10.1 Amplifier with an Un-bypassed Emitter Resistor	384
10.2 Emitter Follower Circuit	388
11. Tuned Voltage Amplifiers	391-414
11.1 Why We Need Tuned Amplifiers	391
11.2 Resonance	393
Series Resonant Circuit, Parallel Resonant Circuit	
11.3 Bandwidth of a Resonant Circuit	398
11.4 Single-tuned Voltage Amplifier	403
Voltage Gain and Frequency Response Curve	
Limitations of Single-Tuned Voltage Amplifiers	
11.5 Double-tuned Voltage Amplifier	405
<i>Summary</i>	407
<i>Check Your Understanding</i>	408
<i>Review Questions</i>	409
<i>Multiple Choice Questions</i>	410

<i>Problems</i>	411
<i>Experimental Exercise</i>	
11.1 Series and Parallel Resonant Circuits	411
12. Sinusoidal Oscillators	415-447
12.1 Why Do We Need an Oscillator	415
12.2 Types of Oscillators	416
12.3 Use of Positive Feedback to Produce Oscillations	416
How an Oscillator Produces Output without any Input	
The Starting Voltage	
12.4 Use of Negative Resistance to Produce Oscillations	418
12.5 The Tank Circuit	419
How to get Sustained Oscillations	
12.6 Tank Circuit (LC) Oscillators	420
Tuned-Collector Oscillator, Hartley Oscillator, Colpitts Oscillator, Clapp Oscillator	
12.7 RC Oscillators	427
RC Phase Lag Circuit, RC Phase Lead Circuit, RC Phase Lead-Lag Circuit	
12.8 RC Phase-shift Oscillator	429
12.9 Wien-bridge Oscillator	430
Working of Wien Bridge Oscillator, Resonant Frequency	
12.10 Crystal Oscillator	433
Piezoelectric Effect, Characteristics of a Crystal, Series and Parallel Resonance of the Crystal, Crystal Oscillator Circuits	
<i>Summary</i>	436
<i>Check Your Understanding</i>	438
<i>Review Questions</i>	439
<i>Multiple Choice Questions</i>	440
<i>Problems</i>	441
<i>Experimental Exercise</i>	
12.1 Hartley Oscillator Circuit	443
12.2 Wien Bridge Oscillator	445
13. Optoelectronic Devices	448-464
13.1 Introduction	448
13.2 Photoelectric Effect	449
13.3 Light-emitting Diode (LED)	450
LED Voltage and Current, LED Brightness	
(1) Seven-Segment Display, (2) Voltage-Polarity Tester	
(3) Continuity Tester	
13.4 Laser Diode	453
13.5 Photodiodes	455
13.6 Phototransistor	456
Phototransistor versus Photodiode	

13.7	Optocoupler	457
13.8	Photoresistor	457
13.9	Photovoltaic Cells	458
13.10	Liquid Crystal Display (LCD)	460
	<i>Summary</i>	461
	<i>Check Your Understanding</i>	462
	<i>Review Questions</i>	463
	<i>Multiple Choice Questions</i>	463
14.	Operational Amplifiers	465-508
14.1	What is an Operational Amplifier	465
	Block Diagram of an OP-AMP, Schematic Symbol of an OP-AMP	
14.2	Ideal Operational Amplifier	467
14.3	The Inverting Amplifier	468
	Virtual Ground, Voltage Gain, Input Resistance	
14.4	The Noninverting Amplifier	469
	Virtual Short, Voltage Gain	
14.5	Some Simple Applications of OP-AMP	470
	Adder or Summing Amplifier, Differential Amplifier, Subtractor, Differentiator, Integrator, Voltage Follower	
14.6	Practical Operational Amplifier	477
	Input Offset Voltage, Input Offset Current, Unity-gain Frequency, Slew Rate, Common-Mode Rejection Ratio (CMRR), Power Supply Rejection Ratio (PSRR)	
14.7	Multivibrators	484
	Bistable Multivibrator	
14.8	Schmitt Trigger Circuit	485
	Transfer Characteristic of Schmitt Trigger Circuit, Hysteresis, Sine-wave to Square-wave Conversion	
14.9	Astable Multivibrators	487
	Square Wave Generator, Triangular Wave Generator, Sawtooth Wave Generator	
14.10	Sample-and-hold (S/H) Circuit	492
	Sampling of Analog Signals, Sample-and-Hold (S/H) Circuit	
	<i>Summary</i>	494
	<i>Check Your Understanding</i>	496
	<i>Review Questions</i>	497
	<i>Multiple Choice Questions</i>	498
	<i>Problems</i>	500
	<i>Experimental Exercise</i>	
14.1	Inverting and Noninverting Op-amp Amplifiers	502
14.2	Op-amp Adder and Buffer Amplifier	504
14.3	Practical Op-amp Integrator Circuit	506

15. Electronic Instruments	509-547
15.1 Introduction	509
15.2 Multimeter	510
The d'Arsonval Movement, Current Measurement, Voltage Measurement, Resistance Measurement Meter Sensitivity (Ohms-per-Volt Rating), Loading Effect	
15.3 Electronic Multimeters	519
15.4 Cathode Ray Oscilloscope (CRO)	521
Cathode Ray Tube (CRT), How a CRO Displays Waveforms, Timebase Voltage, Block Diagram of a CRO, Front Panel Controls of a CRO	
15.5 Applications of CRO	530
(1) Study of Waveforms, (2) Measurement of Voltages, (3) Measurement of Current, (4) Measurement of Frequency, (5) Measurement of Phase Difference	
15.6 Audio Signal Generators	534
Block Diagram of a Signal Generator, Front Panel Controls of a Typical Signal Generator	
<i>Summary</i>	536
<i>Check Your Understanding</i>	538
<i>Review Questions</i>	539
<i>Multiple Choice Questions</i>	540
<i>Problems</i>	542
<i>Experimental Exercise</i>	
15.1 Use of Multimeter	543
15.2 Use of CRO and Signal Generator	544
<i>Index</i>	548

ELECTRONIC DEVICES AND CIRCUITS

The salient features of the book are:

1. The book is a little futuristic. Recently developed semiconductor devices have been discussed, through briefly. Vacuum tubes have been left out altogether.
2. Each Chapter starts with its objectives. The student knows what is expected of him after he goes through the Chapter.
3. Conversational and easy-to-understand language is used. Wherever possible, metaphors are used to explain an idea.
4. Good number of solved examples is given. This helps the student in grasping the idea.
5. The diagrams and illustrations are self-explanatory.
6. The *Summary* given at the end of each Chapter helps in reviewing the whole Chapter in a short time.
7. '*Check Your Understanding*' at the end of each Chapter gives a student a chance to find out how much he has grasped.
8. The *Review Questions* and *Multiple Choice Questions* are helpful to a student in his self-evaluation.
9. The *Problems* (along with their answers) at the end of each Chapter can be used either for the tutorial work in the class, or for the homework.
10. The *Experimental Exercises* give complete guidance to the student to do practical work in the Laboratory.

D.C. Kulshreshtha is presently a Professor in Electronics and Communications Engineering, Jaypee University of Information Technology, Wanknaghat (HP). He earned his B.Tech., with Honours, in Electronics and Electrical Communication Engg., from IIT Kharagpur, and his M.Tech., with Distinction from Delhi College of Engineering, Delhi. For three years, he was at IIT Delhi pursuing research in Digital Signal Processing.

Prof. Kulshreshtha secured 2nd All-India Rank in Indian Engineering Services, and served for five years as Engineer in Wireless Planning and Coordination Wing of Ministry of Communications, Govt. of India.

He has a long teaching experience at Delhi College of Engg. He has authored many excellent textbooks.

ISBN 81-224-1857-0



PUBLISHING FOR ONE WORLD

NEW AGE INTERNATIONAL (P) LIMITED, PUBLISHERS

New Delhi • Bangalore • Chennai • Cochin • Guwahati • Hyderabad
Jalandhar • Kolkata • Lucknow • Mumbai • Ranchi

Visit us at www.newagepublishers.com